

Full Custom Design of **4-Bit Ripple Carry Adder**

VLSI - EEC 433




Spring 2024


By Student:

AbdulRahman Ahmad Hasan AlSindiony


Electronics and Communications Engineering

Alexandria University

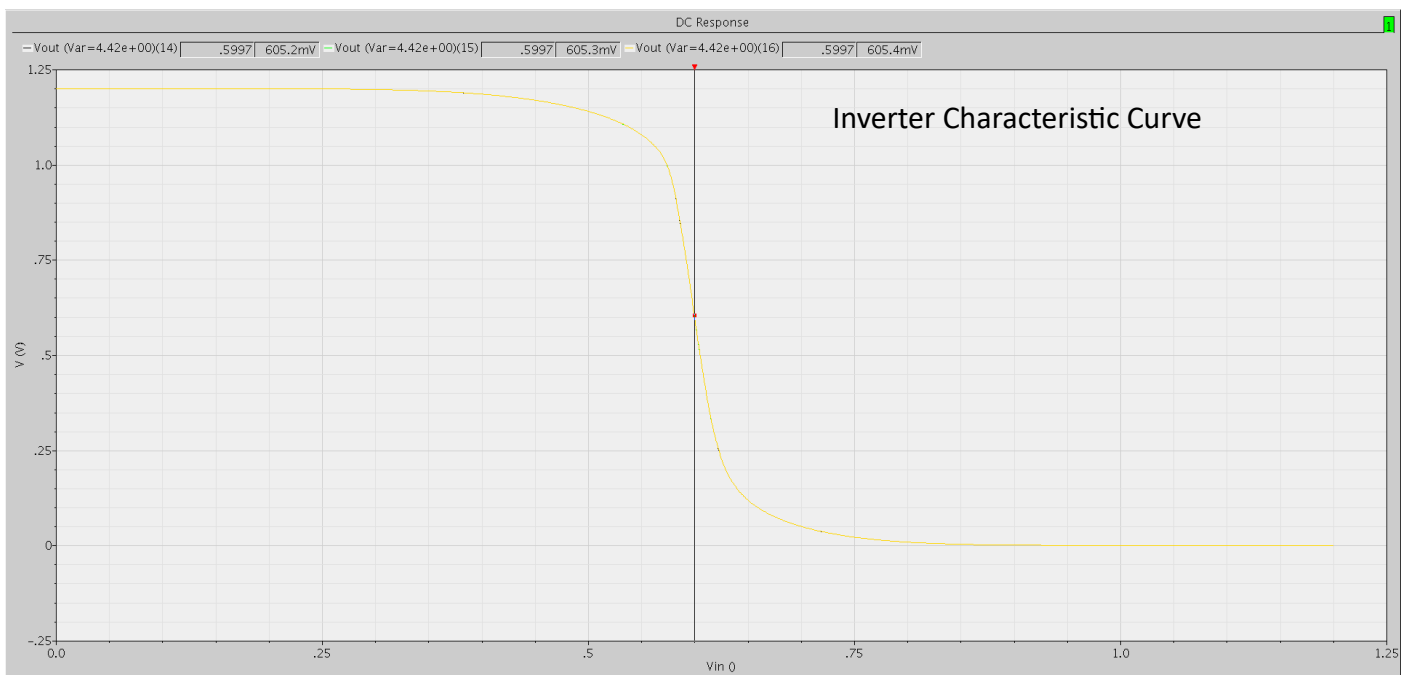 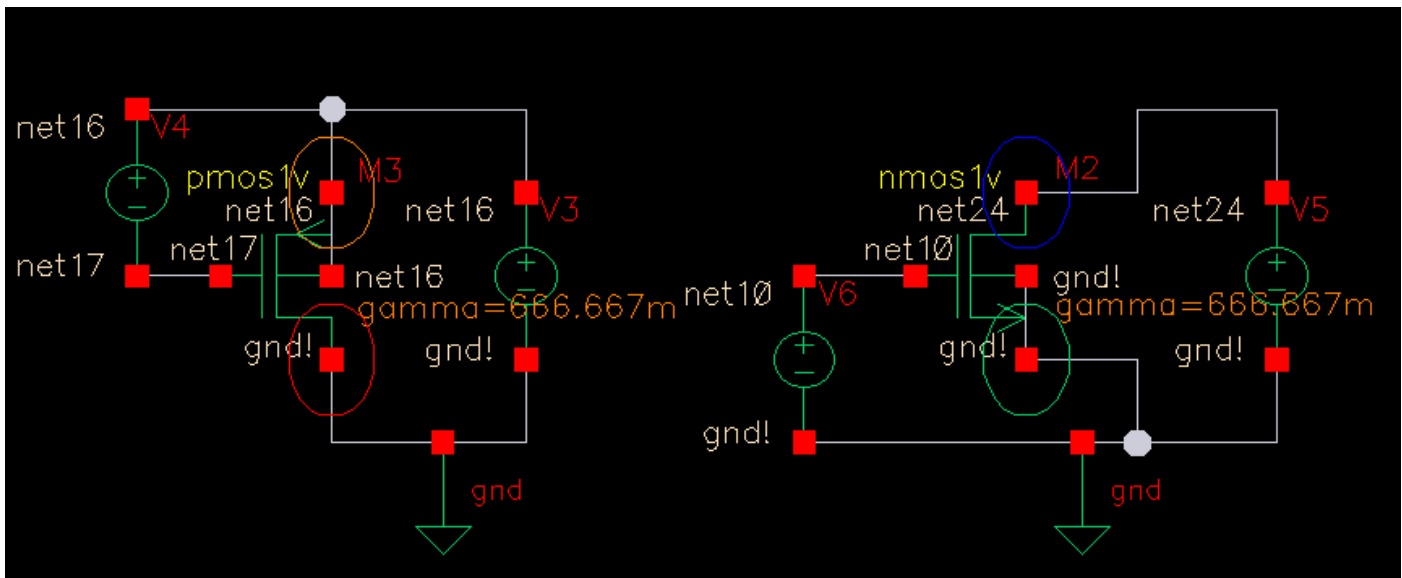


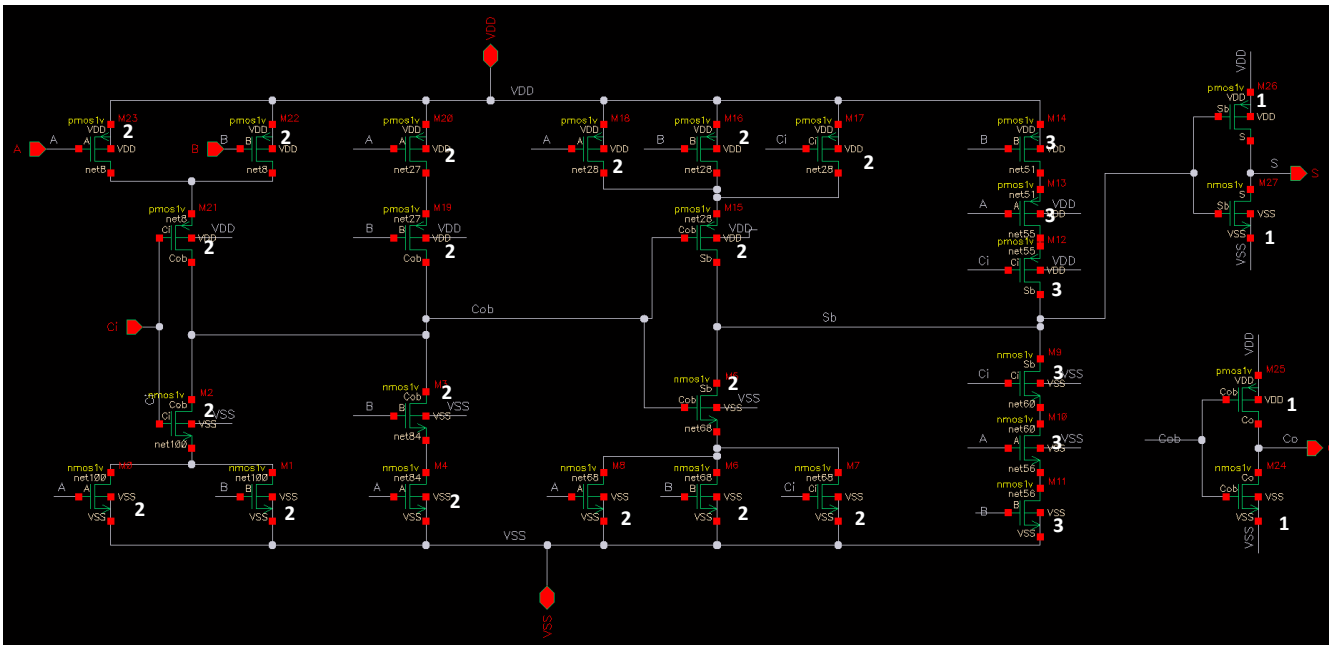


Full Adder Circuit Schematic

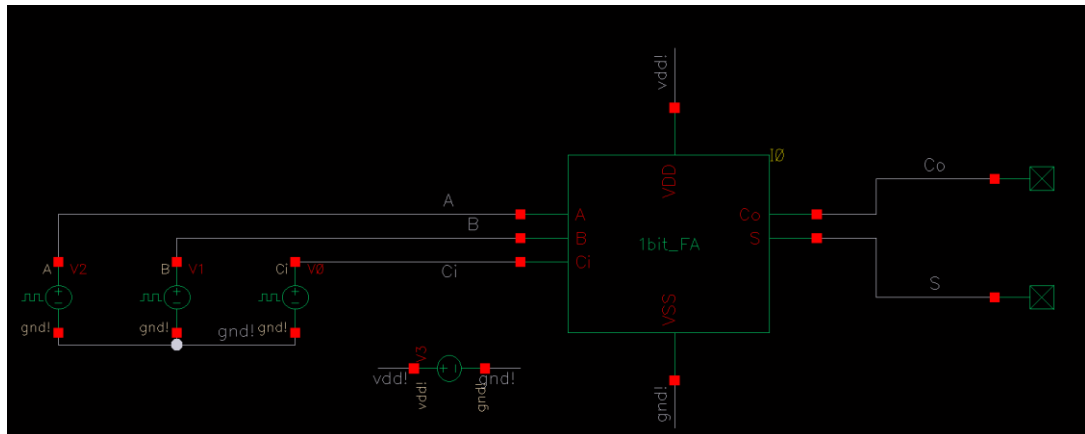



1 bit Full Adder symbol and Test bench

 


Verifying the Functionality of the Full Adder Circuit


Names 	Value
delay(VT("/Co") 0.6 1 "either" V...	-8.664E-11

  Propagation delay for single 1-bit full adder without load = 86.64 pS



Names 	Value
average(abs(i("/V3/PLUS" ?result...	1.552E-5


Power Consumption = 15.5 uW

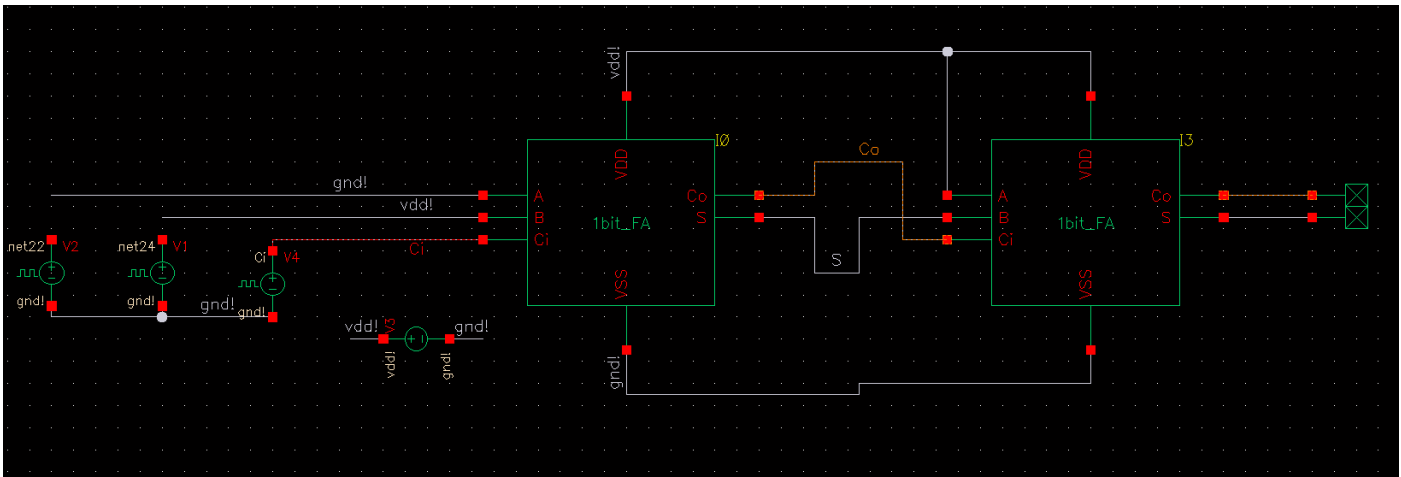


Test bench schematic for calculating the propagation delay with 1 FA Load

Names	Value
delay(VT("/Co") 0.6 1 "either" V...	-1.392E-10

 
Propagation delay for one loaded 1-bit FA = 139.2 pS



 


DC Transfer Characteristics, Changing “ C_{in} ” from 0 to 1.2 V linearly and monitoring “ C_o ”.

 
The mid point is 620 mV, we can redesign for closer point to 600 mV.



 
Circuit Test Bench, with Ideal 4-bit Carry Adder to verify the output of the designed Circuit




Ideal and Practical "Co" signals

 


Ideal and Practical "S0" signals

 

Ideal and Practical "S1" signals

 


Ideal and Practical “S2” signals

 

Ideal and Practical “S3” signals

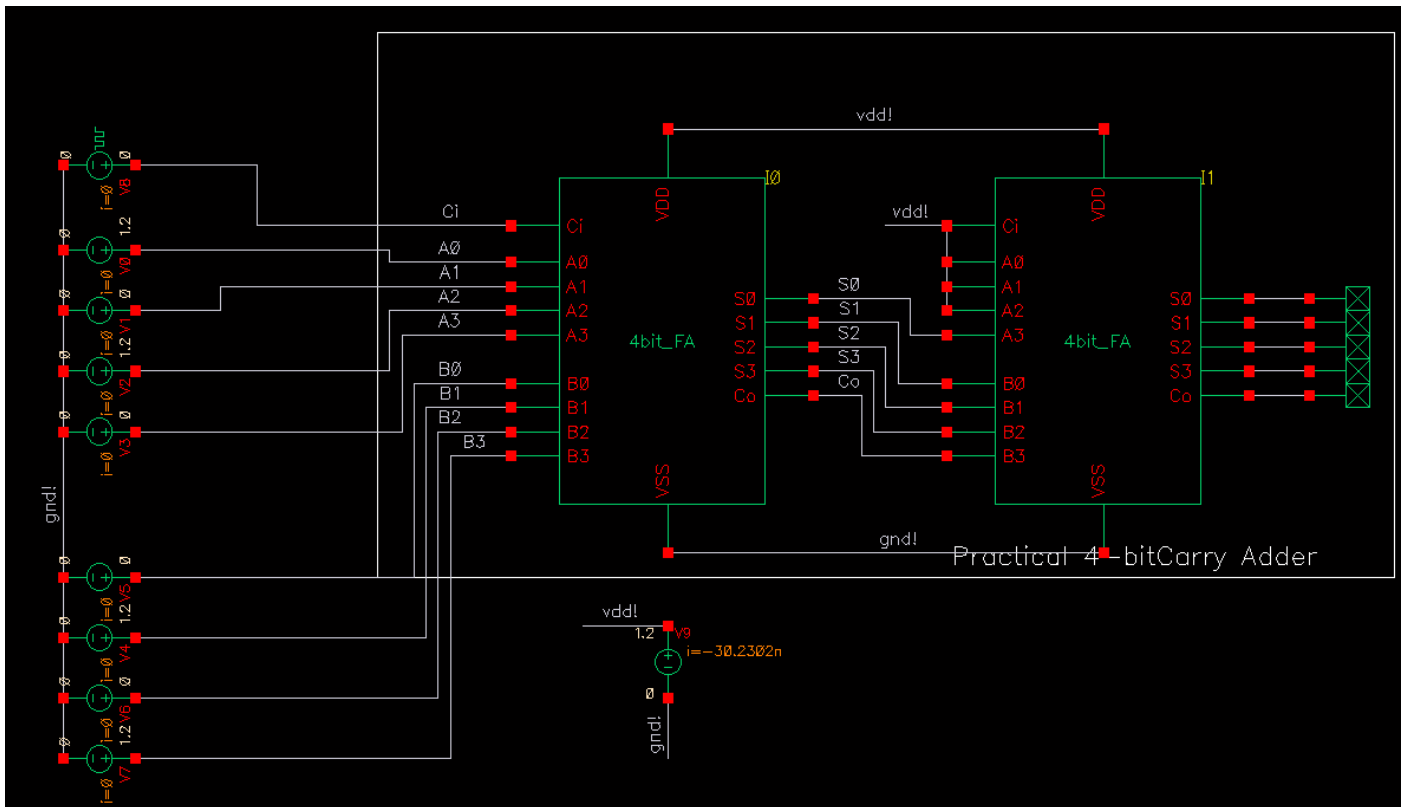
Now we have verified the functionality of the 4-bit ripple carry adder designed circuit.



We have set Ci to 500 MHz clock while A = 0101 , B = 1010, so as to mirror the input carry to the output carry.


Names	Value
delay(VT("/Ci") 0.6 1 "either" VT...	6.622E-10

 Propagation Delay of the 4-bit ripple adder between Ci and Co of the final stage = 662.5 pS



Names	Value
frequency(VT("/Co"))	5.0E8

500 MHz output Carry

 

Input/Output Transfer Characteristics for Ci to Co

CONCLUSION**Transistor Sizing for a single bit FA:**

- 2 Inverters each one with PMOS (1105n/130n) and NMOS (250n/130n)
- 3 Stacked PMOS transistors with (3*1105n/130n)
- 3 Stacked NMOS transistors with (3*250n/130n)
- 9 transistors for the rest of PUN (Pull Up Network) with (2*1105n/130n)
- 9 transistors for the rest of PDN (Pull Down Network) with (2*250n/130n)

With total number of 28 Transistors for a single cell.

Area Estimation:

PMOS: $(9*2 + 3*3 + 2*1) * 1105n * 130n = 4.1658 \text{ um}^2$ without routing

NMOS: $(9*2 + 3*3 + 2*1) * 250n * 130n = 0.9425 \text{ um}^2$ without routing

Approximate area could be = $1.5 * (4.1658 + 0.9425) = 7.6625 \text{ um}^2$ for a single 1 bit FA

Total approximate area = $4 * 7.6625 = 30.65 \text{ um}^2$


Propagation Delay: 662.5 pS

Power Consumption: 373.2 uW

Technology: 130 nm (min Length), 150 nm (min Width)


Following We will exploit the inverting property where “Inverting all the inputs of a full-adder cell also inverts all the outputs”. This should exclude the extra inverters we added in the odd cells.
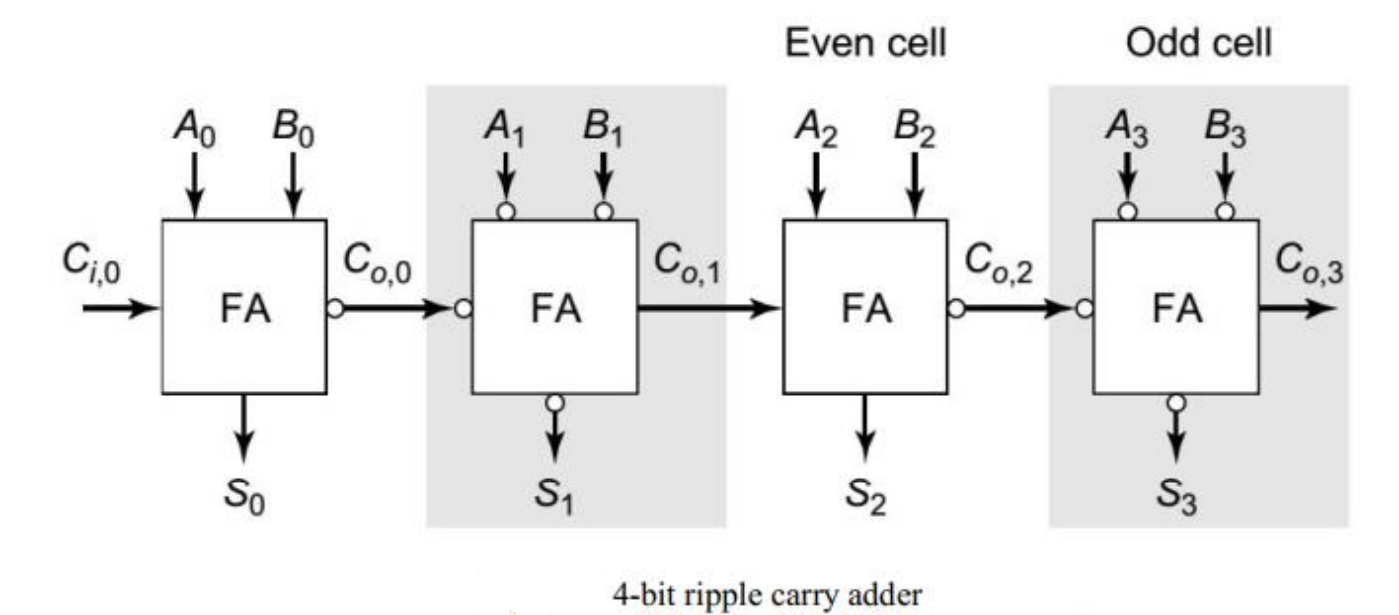
$$\overline{A'.B' + C'_i(A' + B')} \rightarrow \text{solves to } \rightarrow A.B + C_i(A + B) = C_o$$




Inverter Symbol	Inverter Schematic


$$W_p = 1105n, W_n = 250n$$

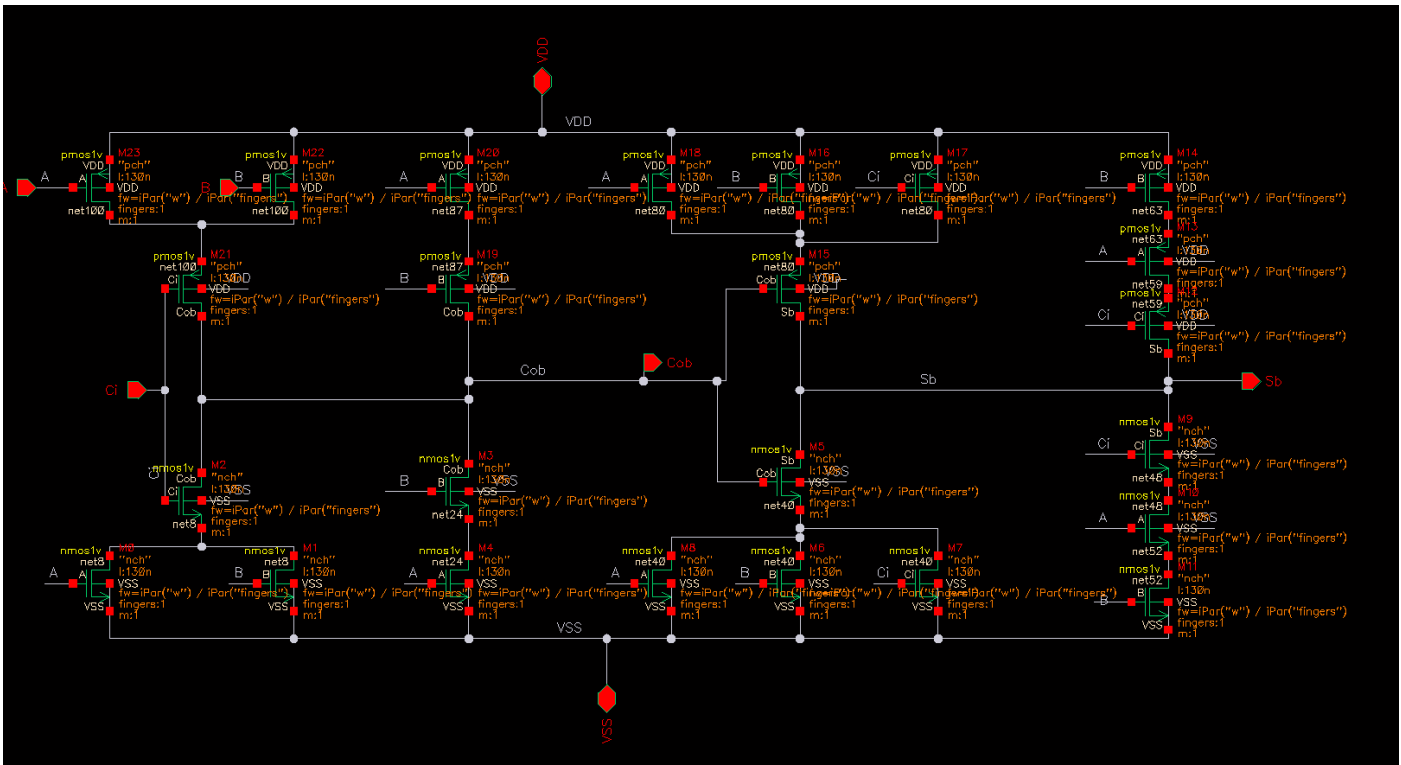

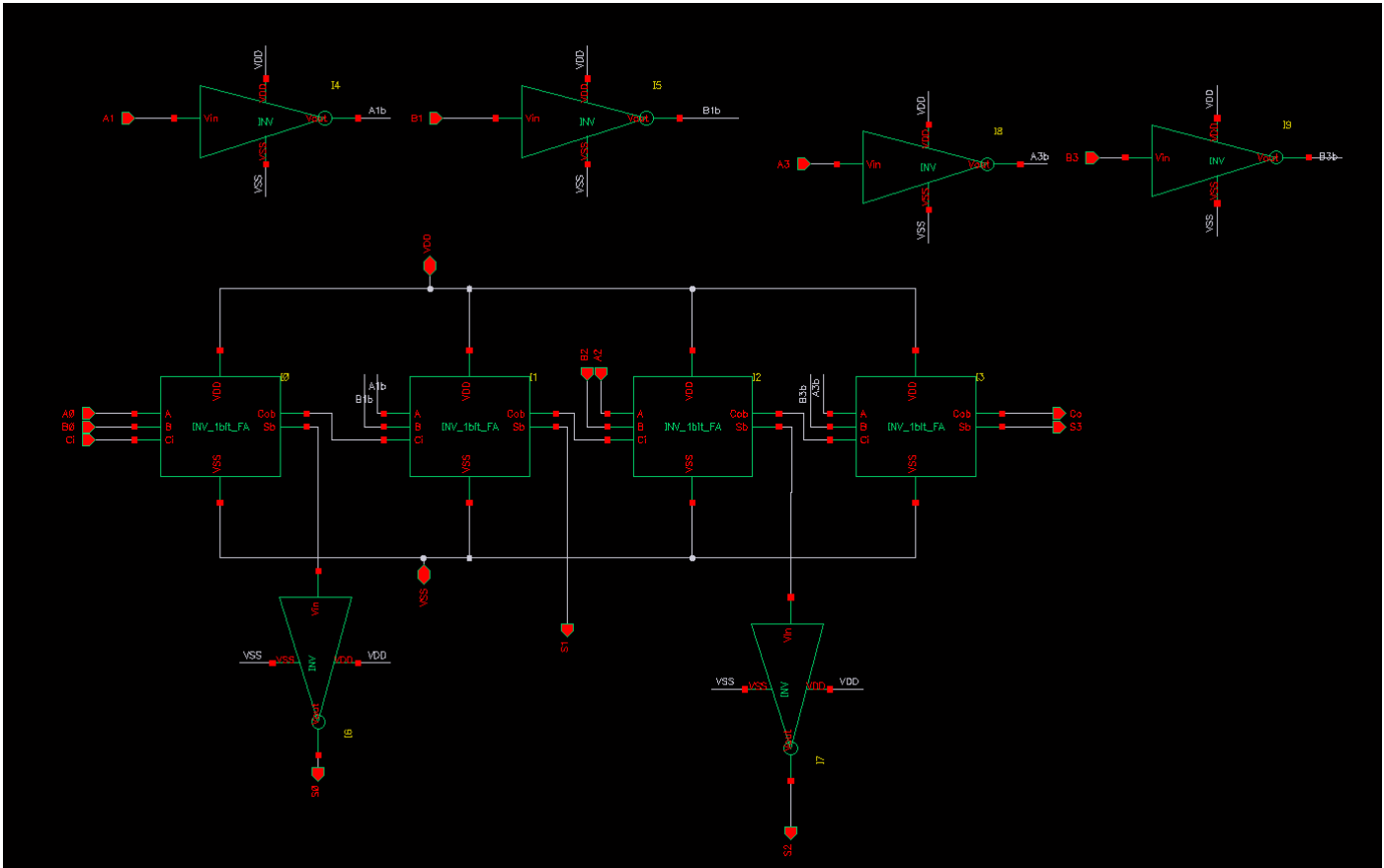
New Schematic for the single FA cell with inverted outputs without extra inverters



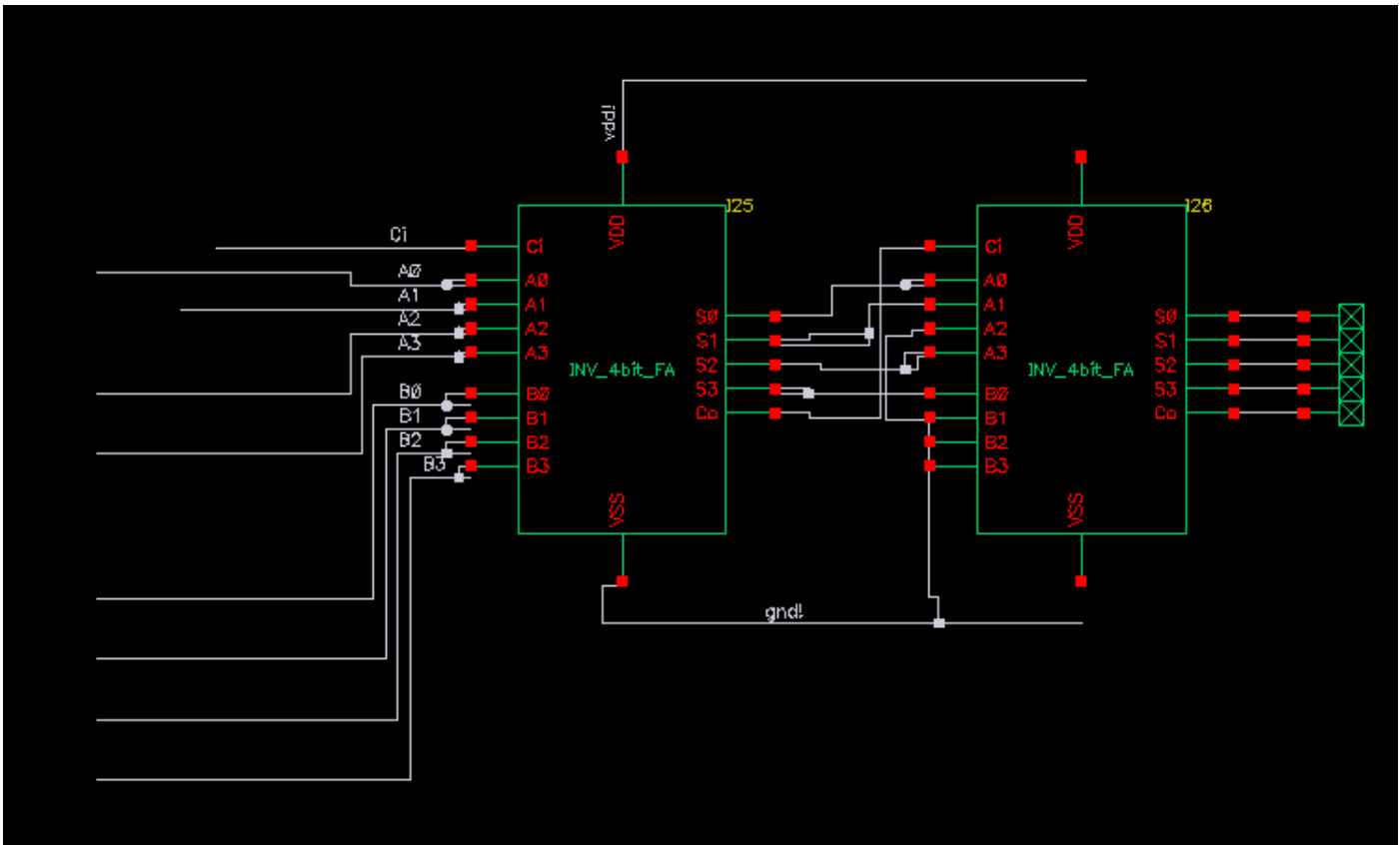
The Connections of the inverters, reducing the total inverter count by two and reducing the inverters at the critical path by 4.




The New Design Test Bench

 


Ideal and Practical "Co" signals

 


Voltage Transfer Characteristics

 


Ideal and Practical "S0" signals

 

Ideal and Practical “S1” signals

 


Ideal and Practical “S2” signals

 

Ideal and Practical "S3" signals


pwr 304.2u

 Power consumption for the second design = 304.2 uW



difference Delay 138.3p

 The delay Difference between the two designs of 4-bit ripple carry adder = 138.3 pS



The propagation delay of the second design = 526.17 pS

CONCLUSION

Transistor Sizing for a single bit FA:

- 3 Stacked PMOS transistors with (3*1105n/130n)
- 3 Stacked NMOS transistors with (3*250n/130n)
- 9 transistors for the rest of PUN (Pull Up Network) with (2*1105n/130n)
- 9 transistors for the rest of PDN (Pull Down Network) with (2*250n/130n)

With total number of 24 Transistors for a single cell.

In addition to another 6 Inverters for connections each one with PMOS (1105n/130n) and NMOS (250n/130n)

Area Estimation:

PMOS: $(9*2 + 3*3) * 1105n * 130n = 3.87855 \text{ um}^2$ without routing

NMOS: $(9*2 + 3*3) * 250n * 130n = 0.8775 \text{ um}^2$ without routing

Approximate area could be = $1.5 * (3.87855 + 0.8775) = 7.134 \text{ um}^2$ for a single 1 bit FA

Total approximate area = $4 * 7.134 + 6*(1.105+0.250)*0.130*1.5 = 30.12 \text{ um}^2$

Propagation Delay: 526.17 pS

Power Consumption: 304.2 uW

Technology: 130 nm (min Length), 150 nm (min Width)